


絶縁型コンバータ

電気電子工学専攻
鵜野 将年


Outline

1. Why Isolation?
2. Isolated Converter Applications
3. Isolated Converters
4. Primary- and Secondary-Side Topologies
5. Soft Switching in Isolated Converters
6. Fundamental Operation (Waveforms and Current Flows)


Why Isolation?

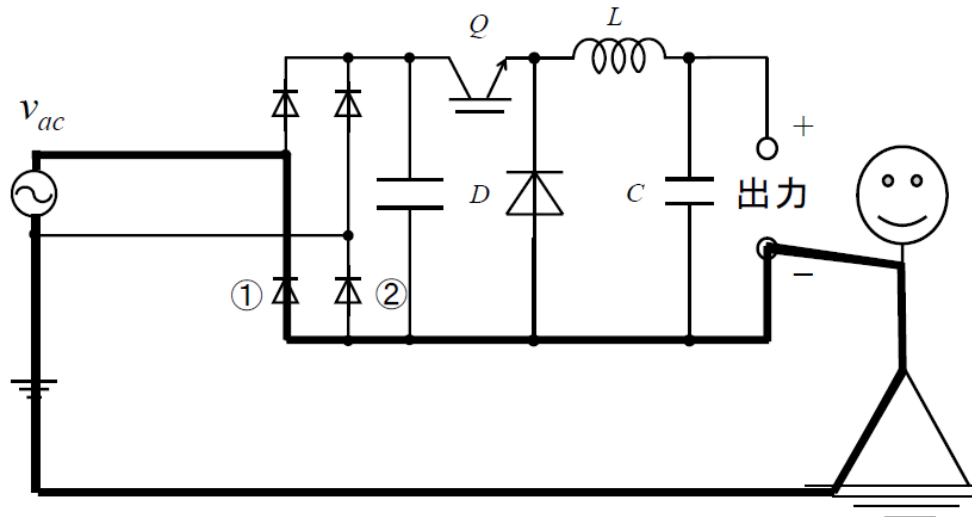

Without Isolation

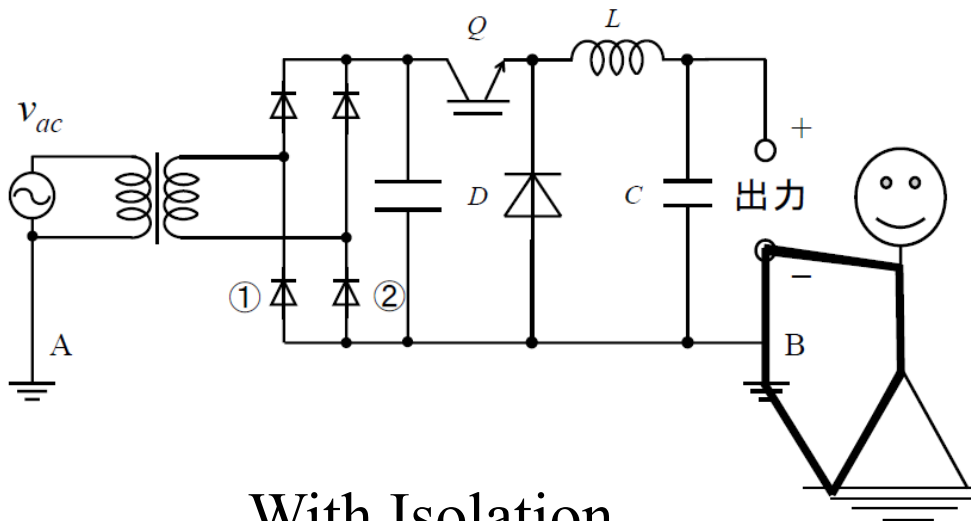


With Isolation

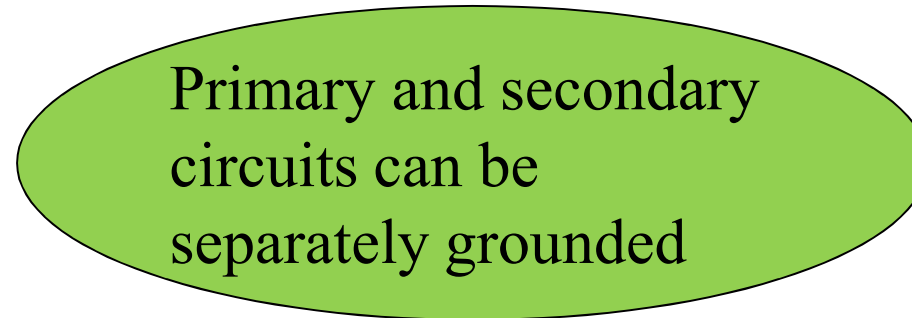

Isolated Converter Applications

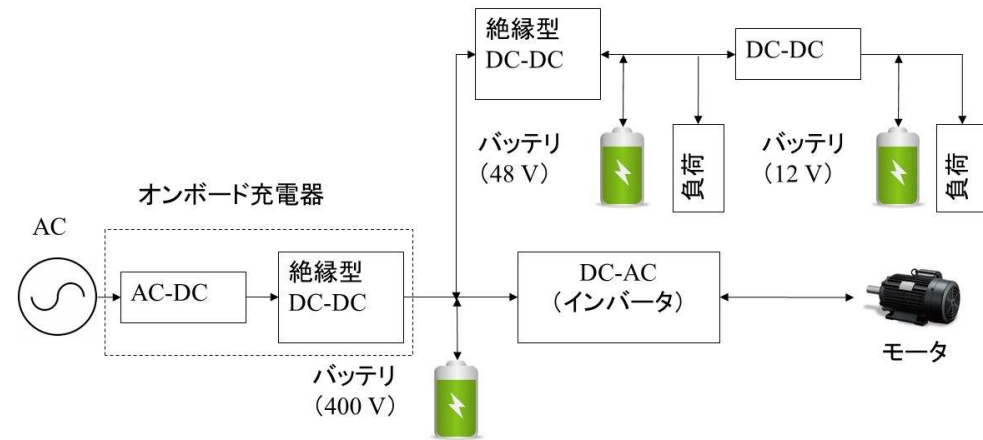
- Home appliance
- Electric vehicle
- Renewable energy
- etc.



Electric Vehicle Power System Example




Isolated Converters

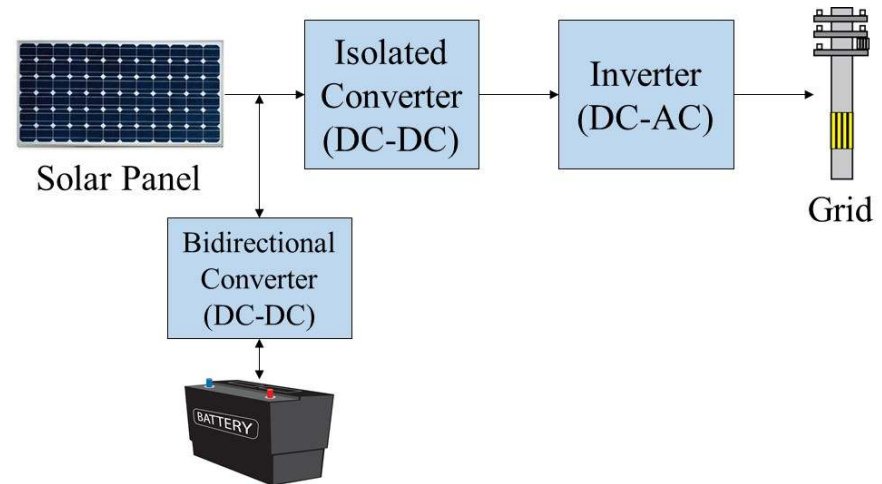


Grid-Connected PV System Example


Isolated Converters

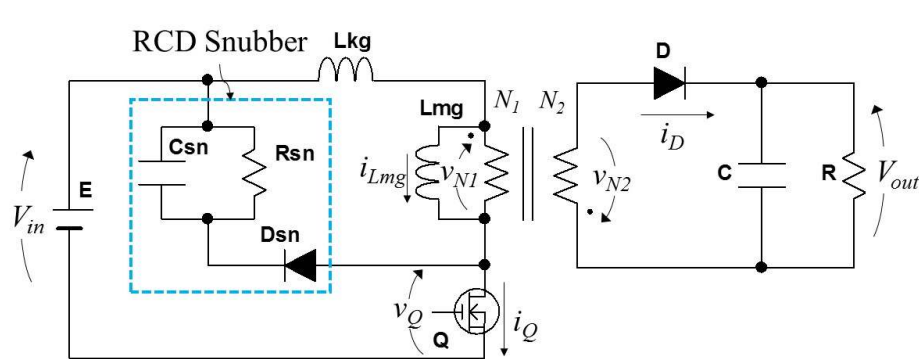


Flyback Converter

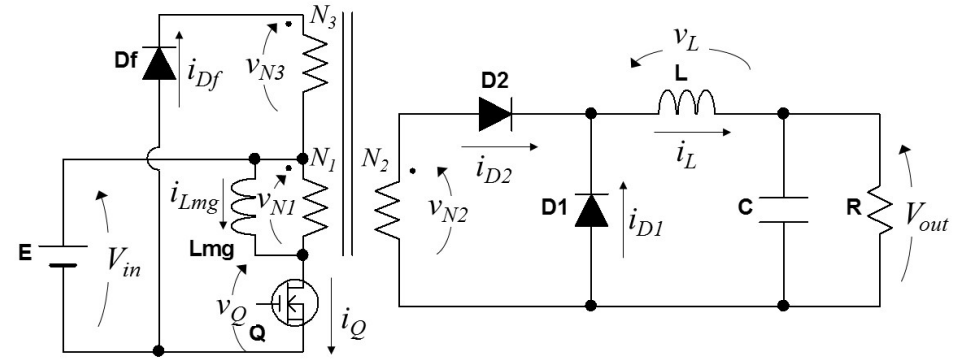

Forward Converter

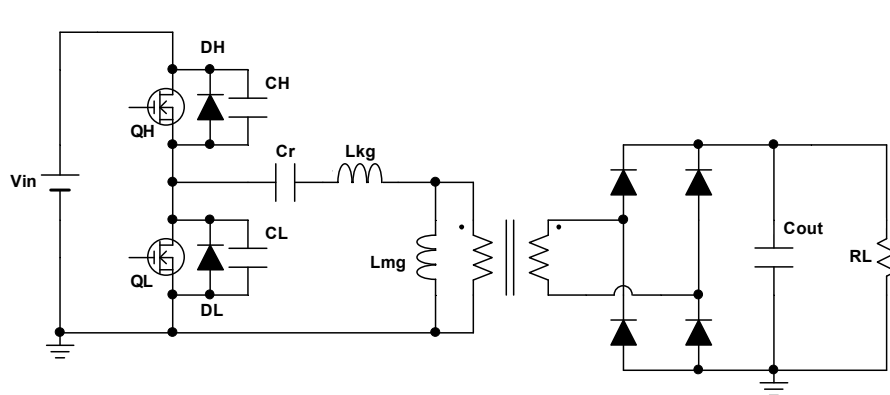

Resonant Converter
(LLC Converter)

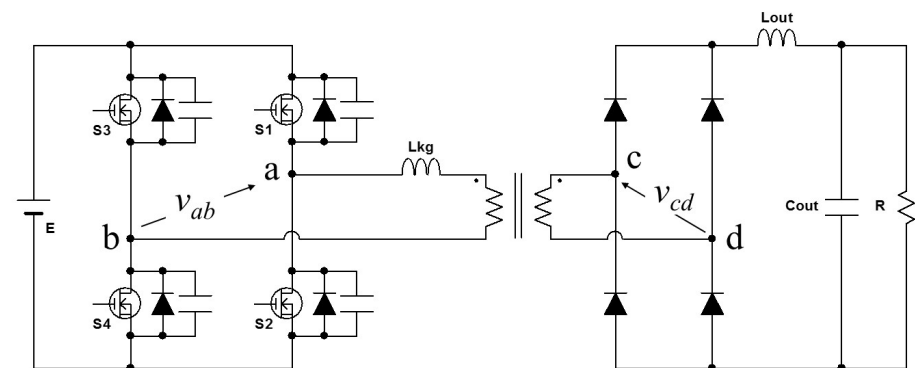


Full-Bridge Converter

Isolated Converter Topology

Primary Side
(Square-Wave Generator)

High-Frequency
Transformer


Secondary Side
(Diode Rectifier)

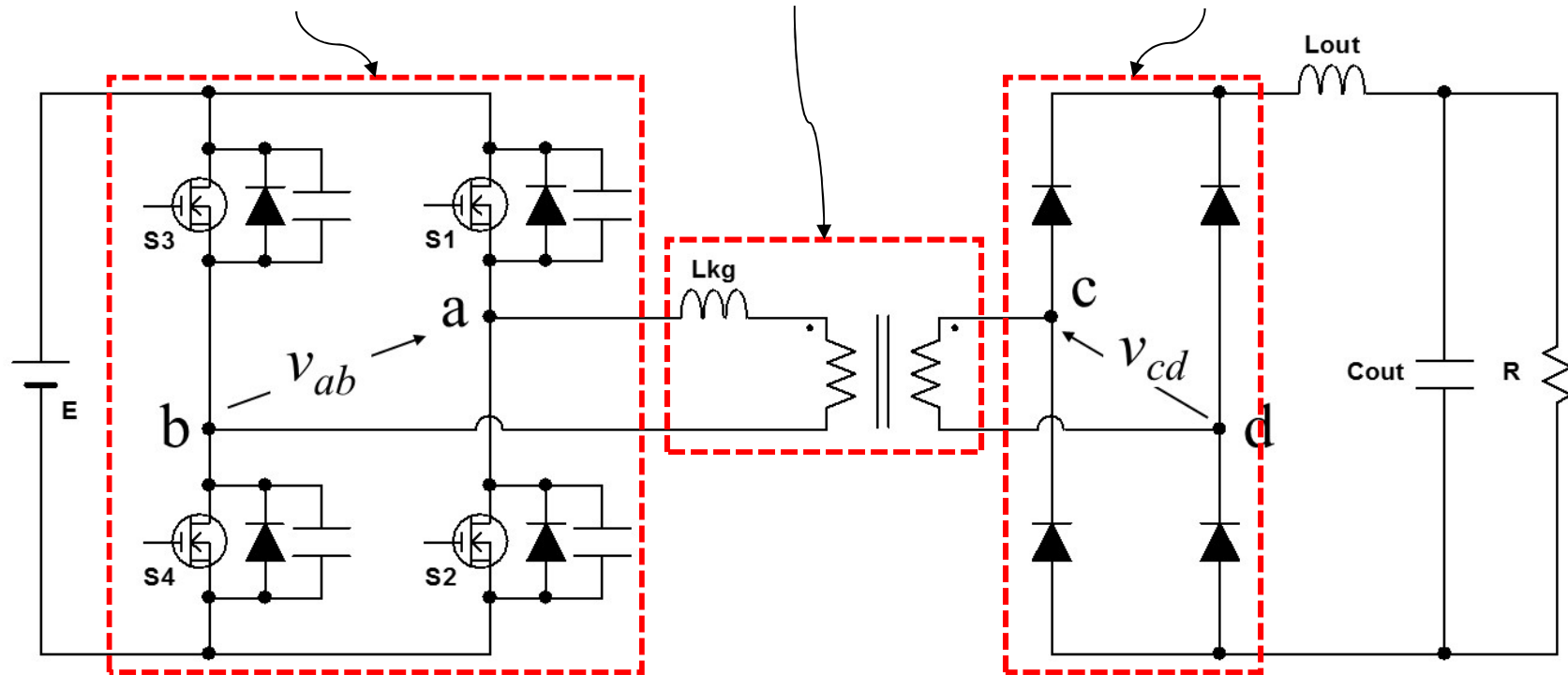


Full-Bridge Converter (with Full Bridge Diode Rectifier)

Combination of primary- and secondary-side circuits with high-frequency transformer in between

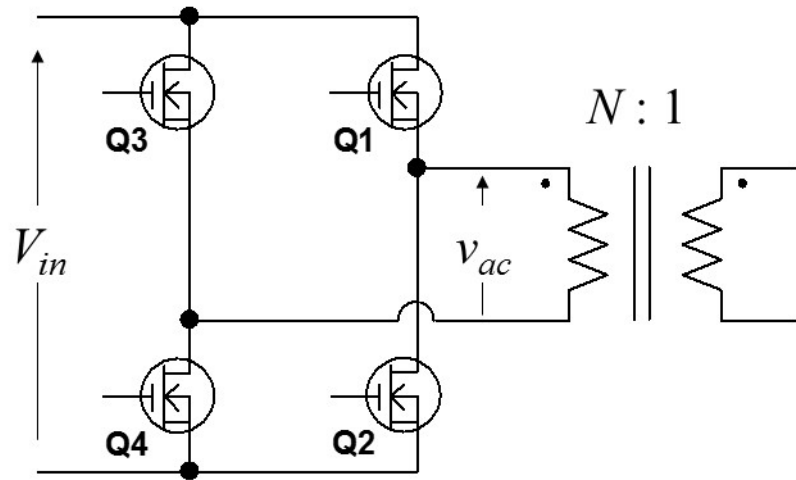
Primary-Side Topologies for Isolated Converters




Full-Bridge

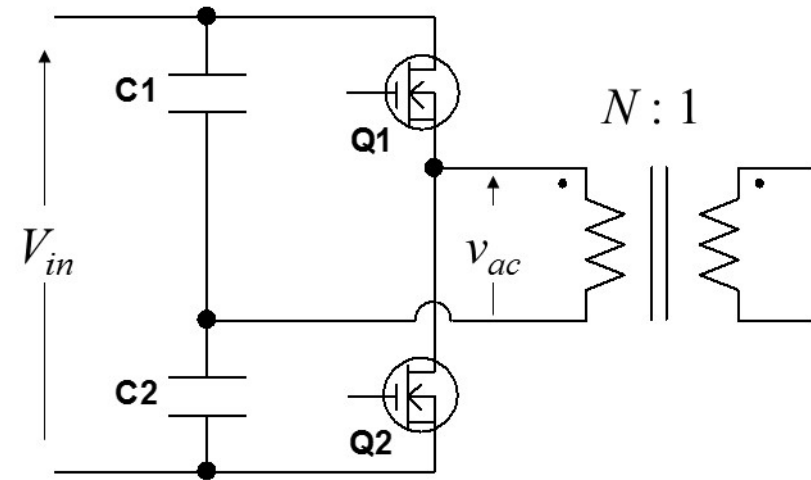

Half-Bridge

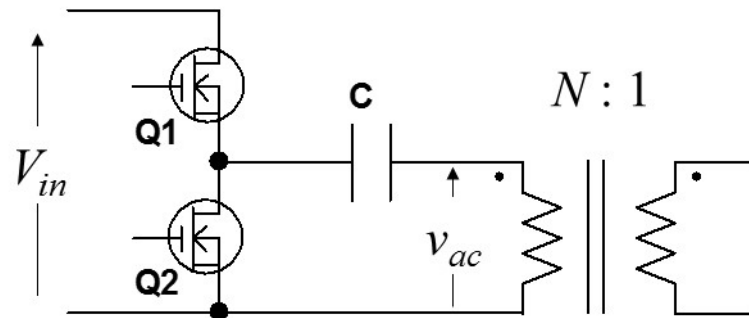



Asymmetric Half-Bridge (AHB)

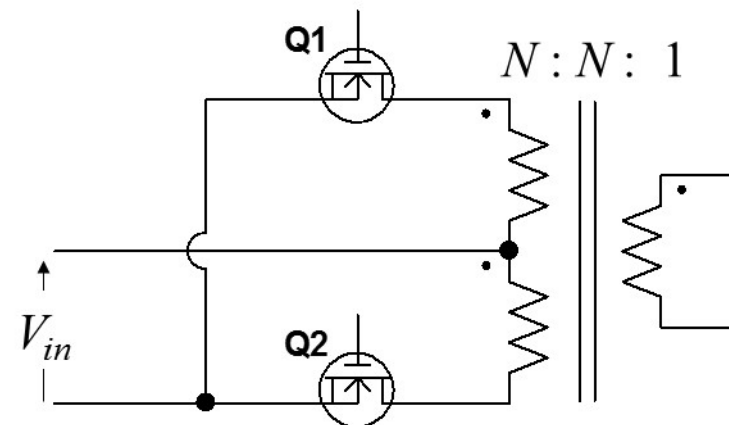

Push-Pull



Primary Side Operations (Full- and Half-Bridges)

Full-Bridge

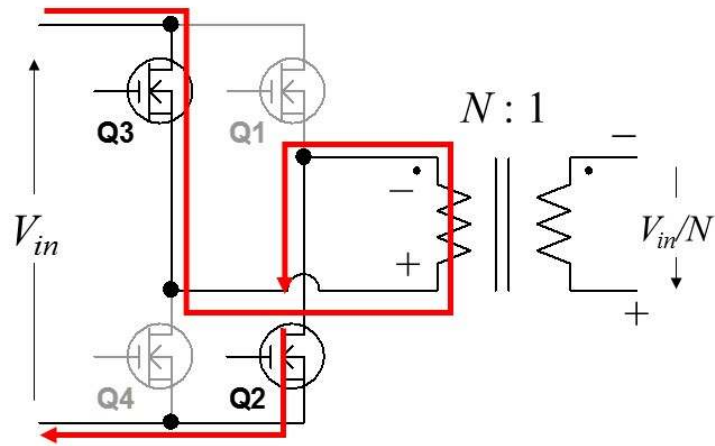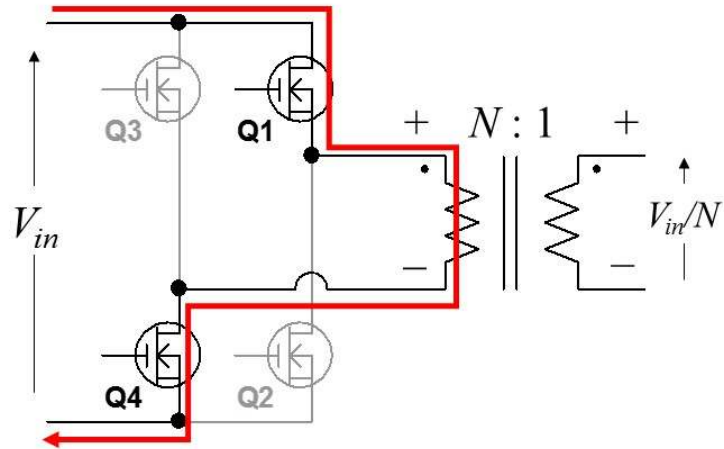

Output is $\pm V_{in}/N$



Half-Bridge

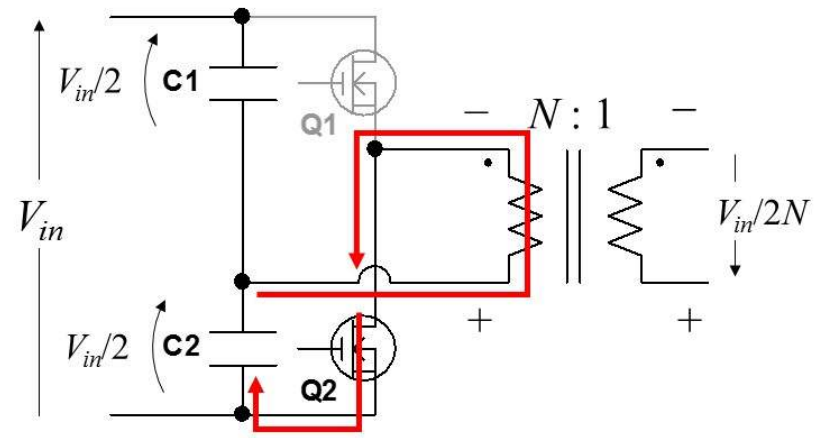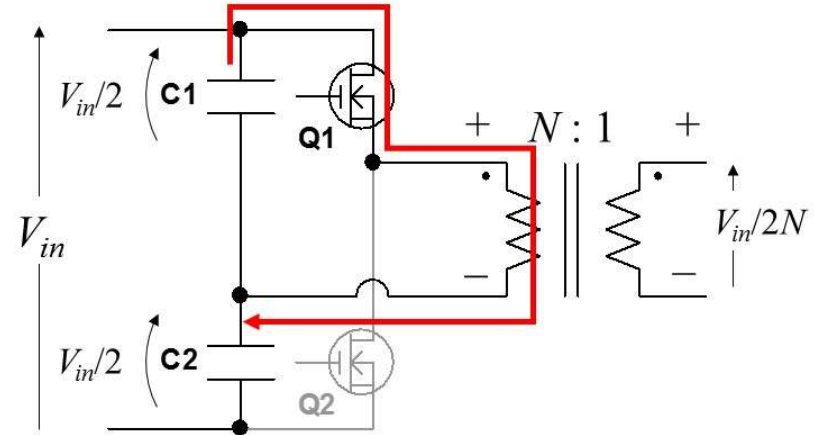

Output is $\pm V_{in}/2N$

Primary Side Operations (AHB and Push-Pull)

Asymmetric Half-Bridge

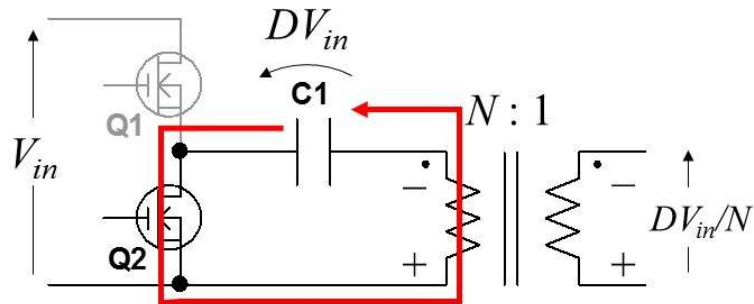
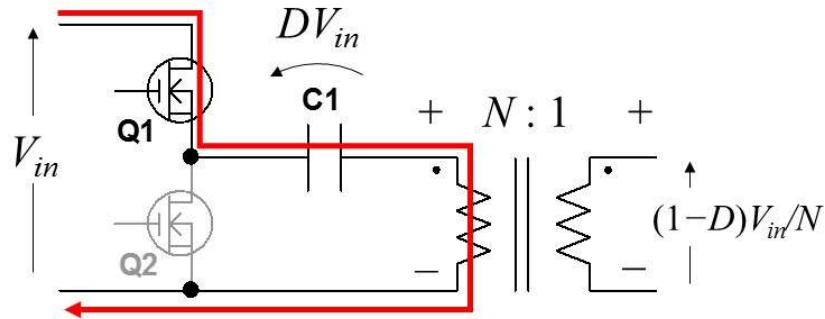


D : Duty cycle of Q_1

Voltage of C_1 is DV_{in} because the average winding voltage must be 0 under steady-state conditions


Output is $+(1-D)V_{in}/N$ and $-DV_{in}/N$

Push-Pull

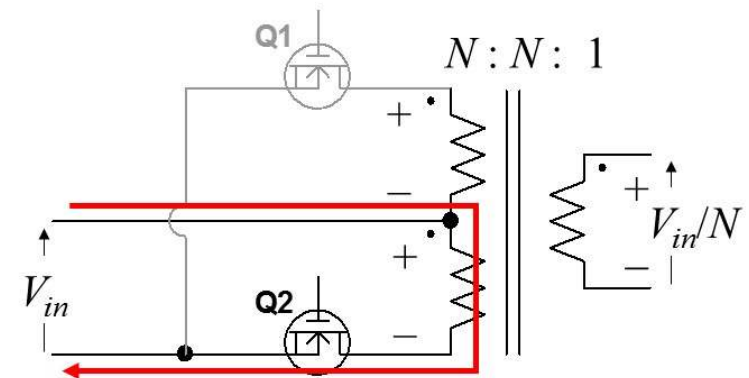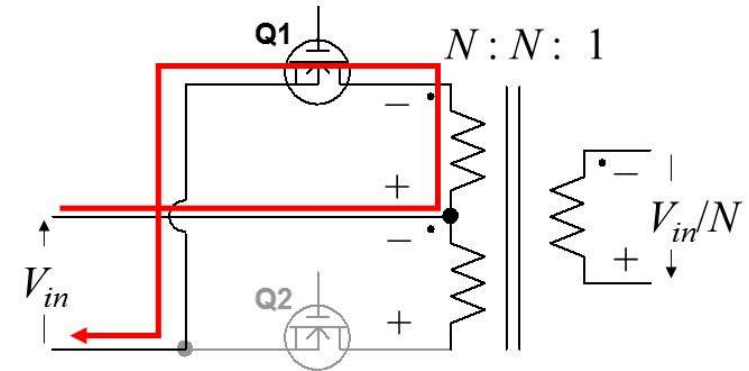


Output is $\pm V_{in}/N$

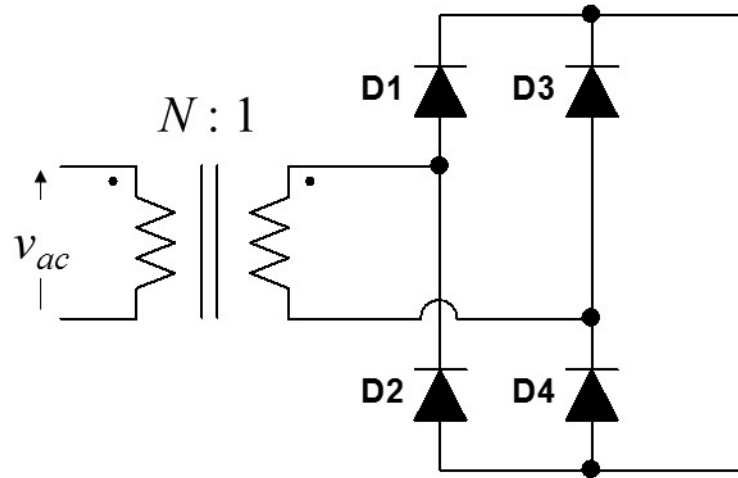
Secondary-Side Topologies for Isolated Converters




Full-Bridge Rectifier

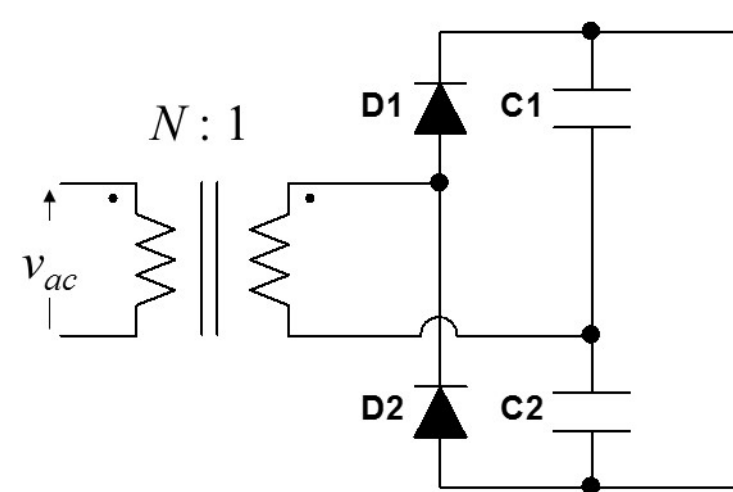

Doubler

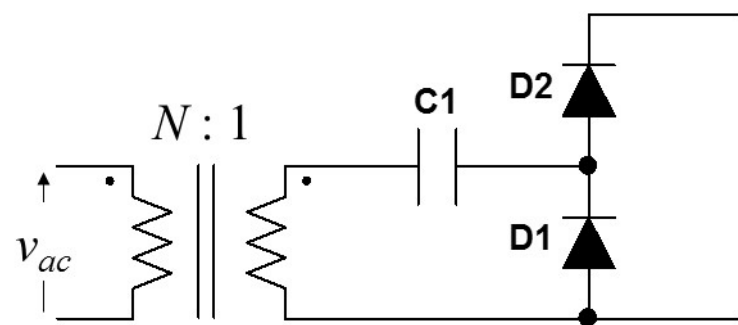



Doubler

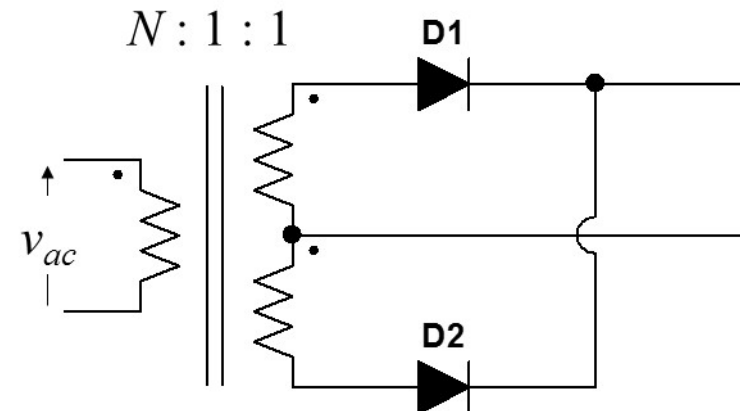

Center-Tap Rectifier



Secondary Side Operations (Full Bridge and Doubler)

Full-Bridge

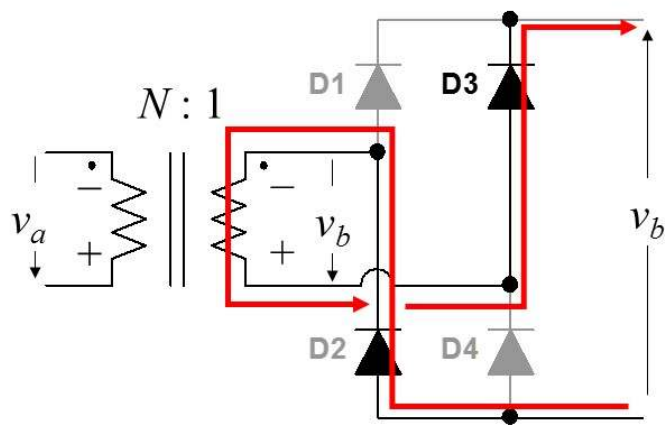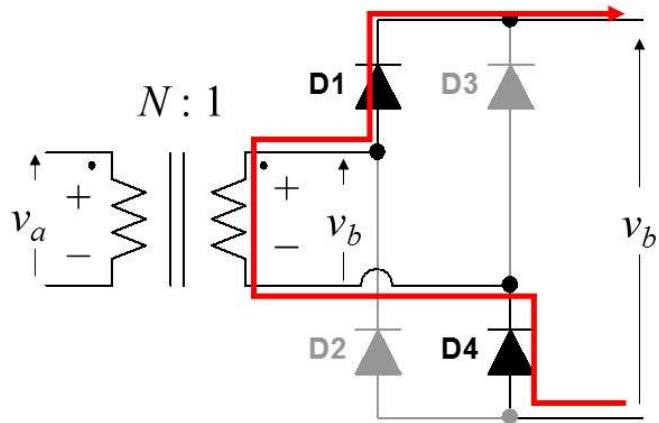

Output is v_b



Doubler

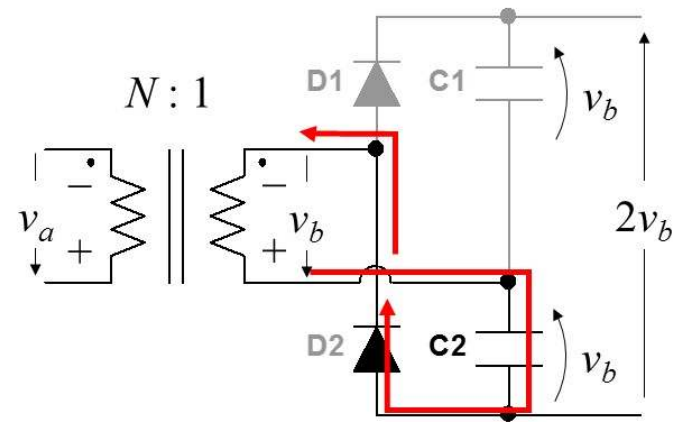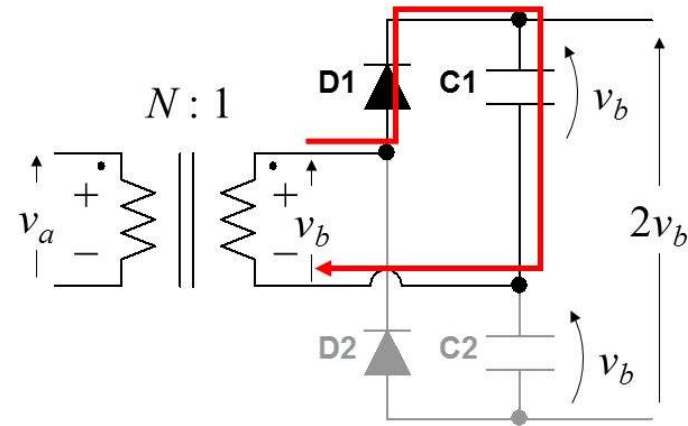

Output is $2v_b$



Secondary Side Operations (Doubler and Center-Tap)

Doubler

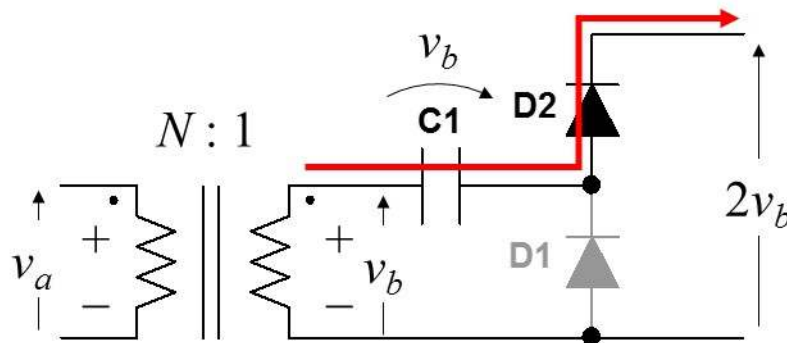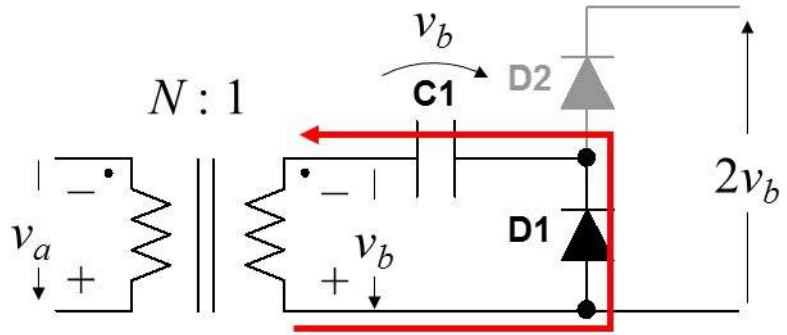



Output is $2v_b$

Center-Tap

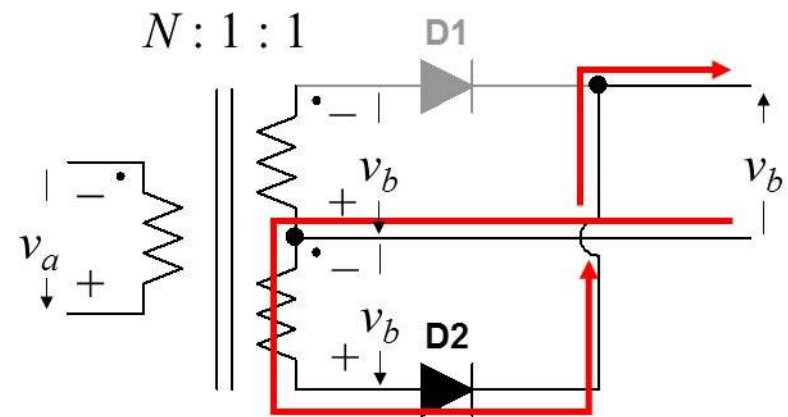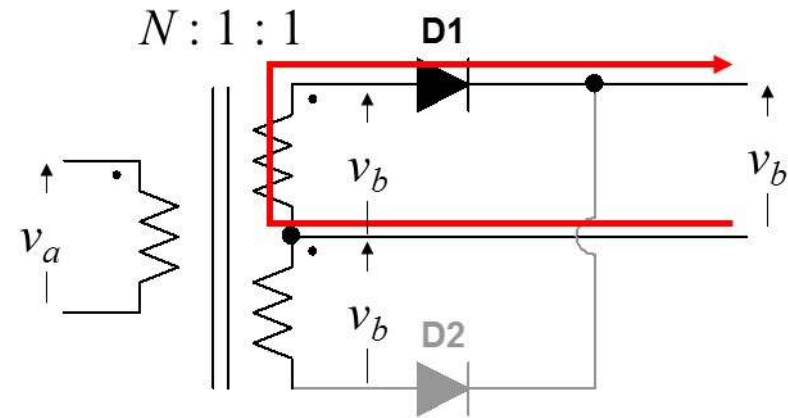


Output is v_b


Switching Transitions of Isolated Converter

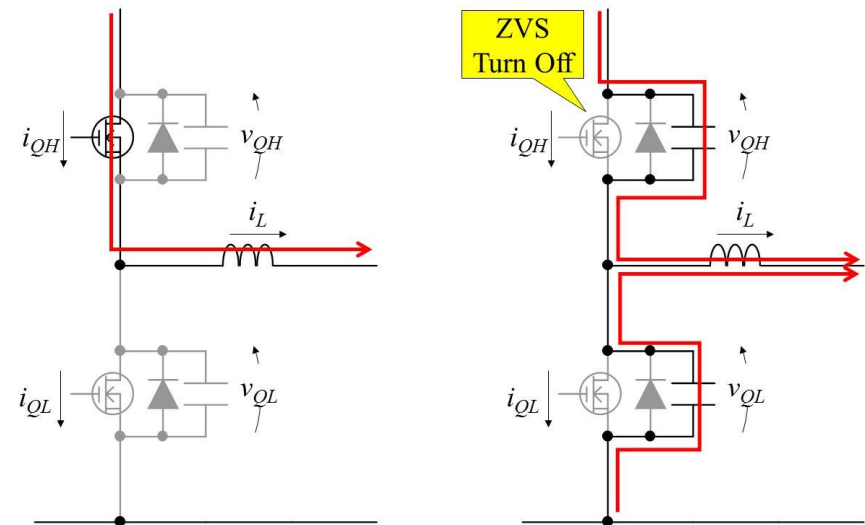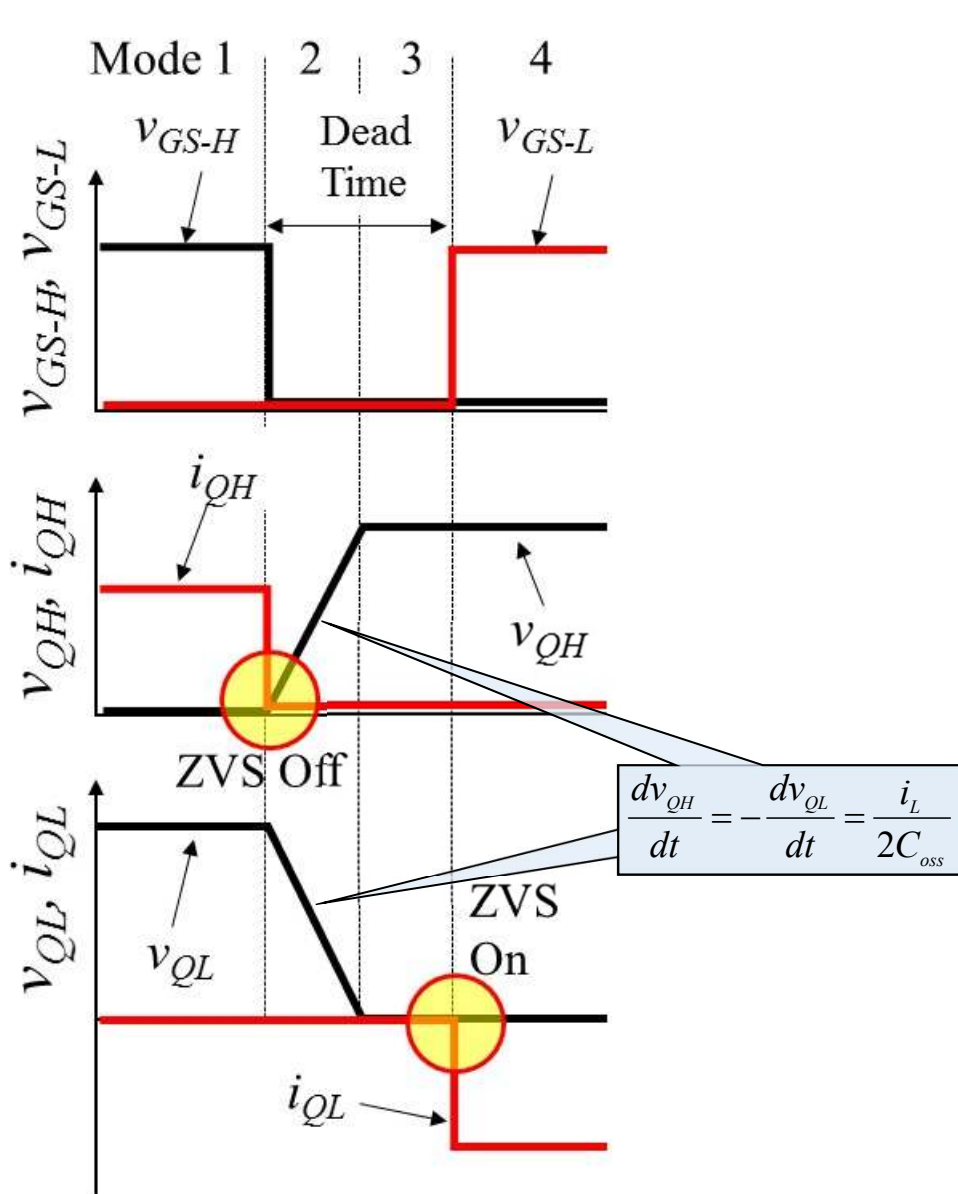


Mode 1

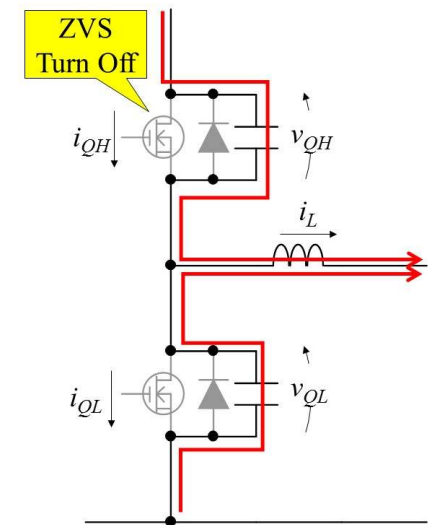

Mode 2


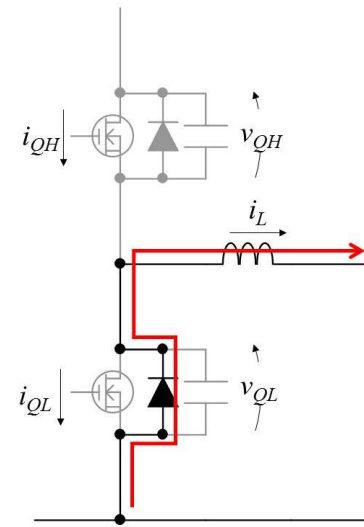


Mode 3

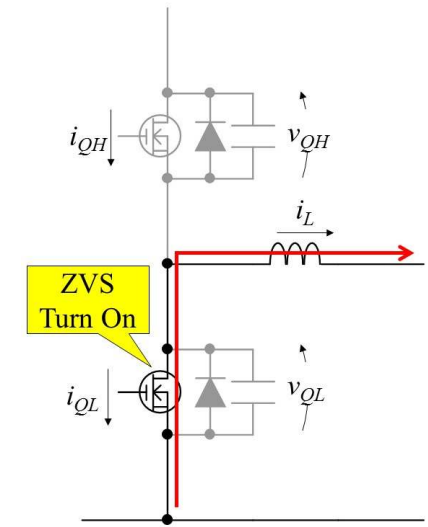


Mode 4


Switching Transitions of Isolated Converter

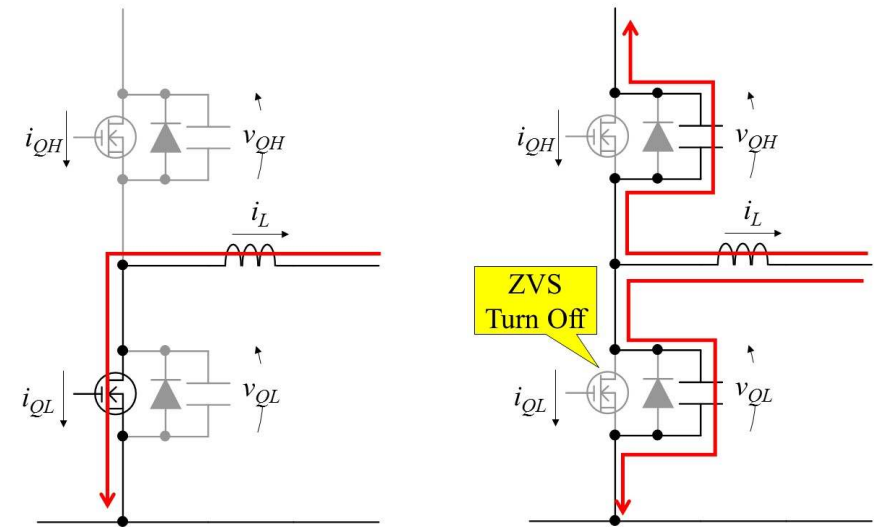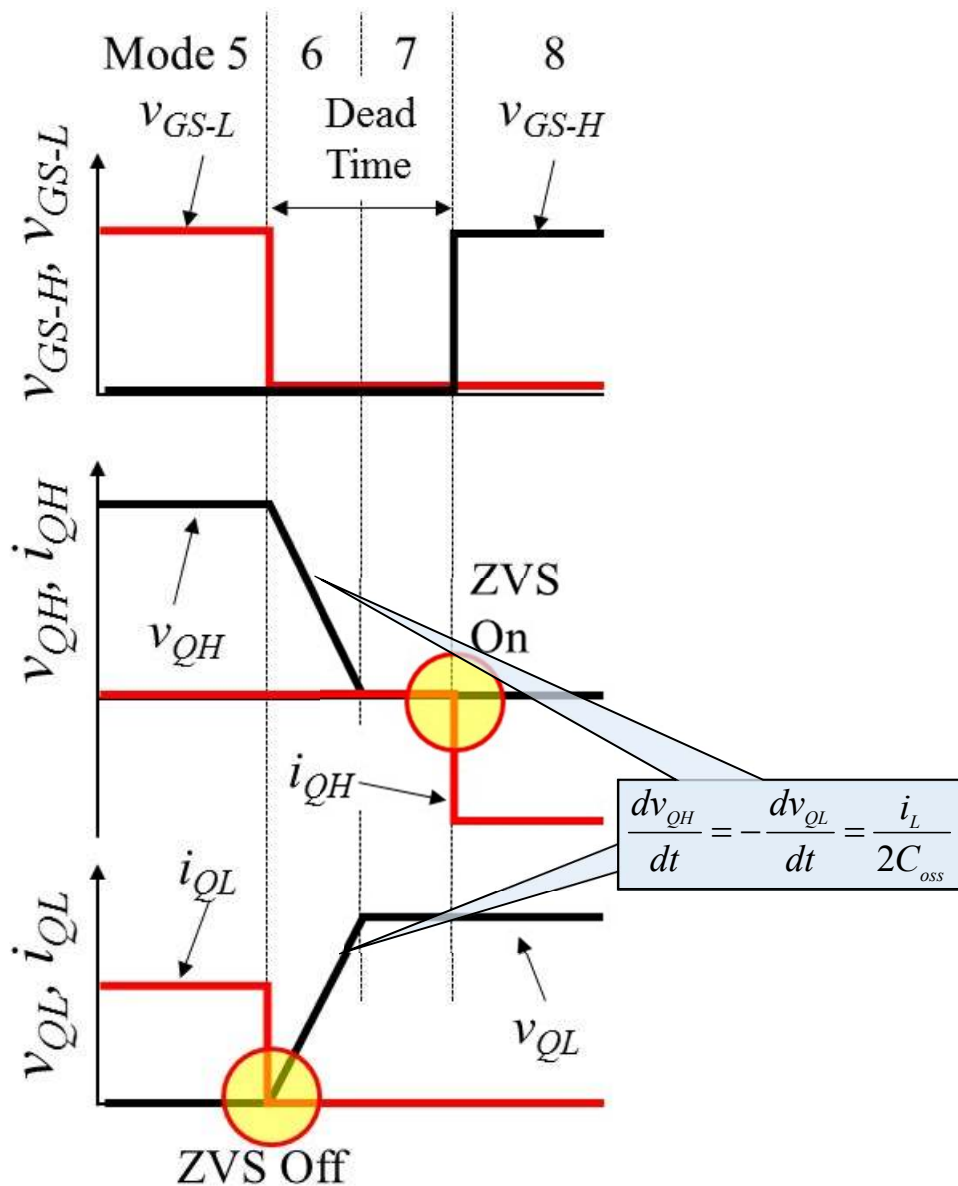


Mode 5

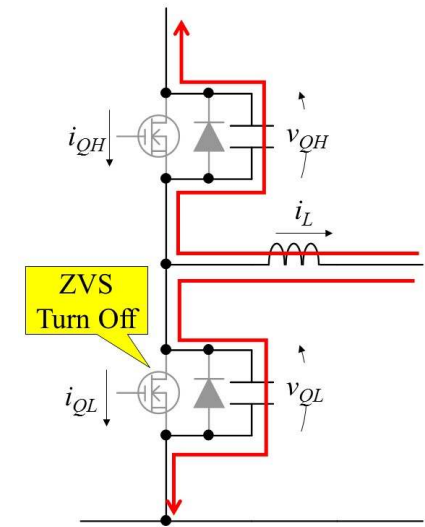

Mode 6


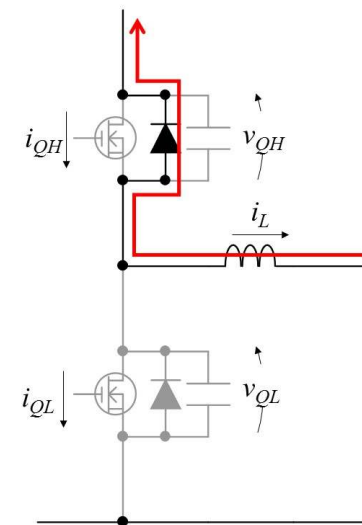


Mode 7

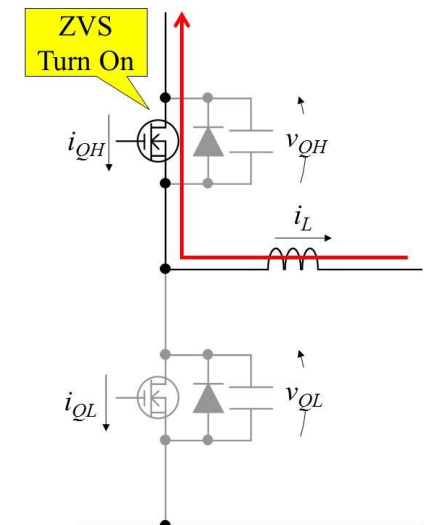


Mode 8

Switching Transitions of PWM Buck Converter

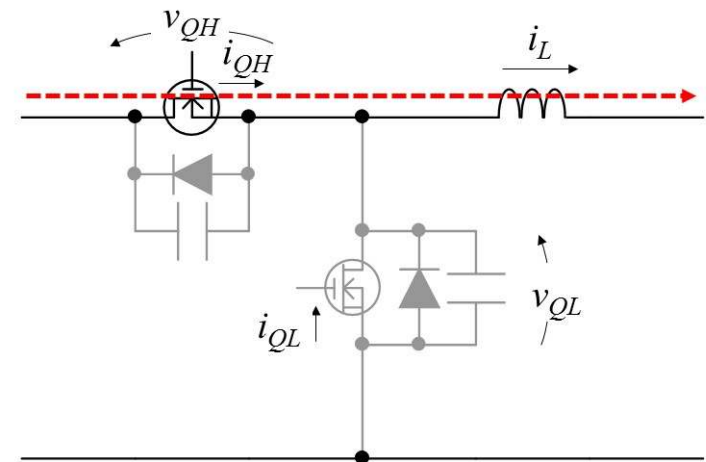
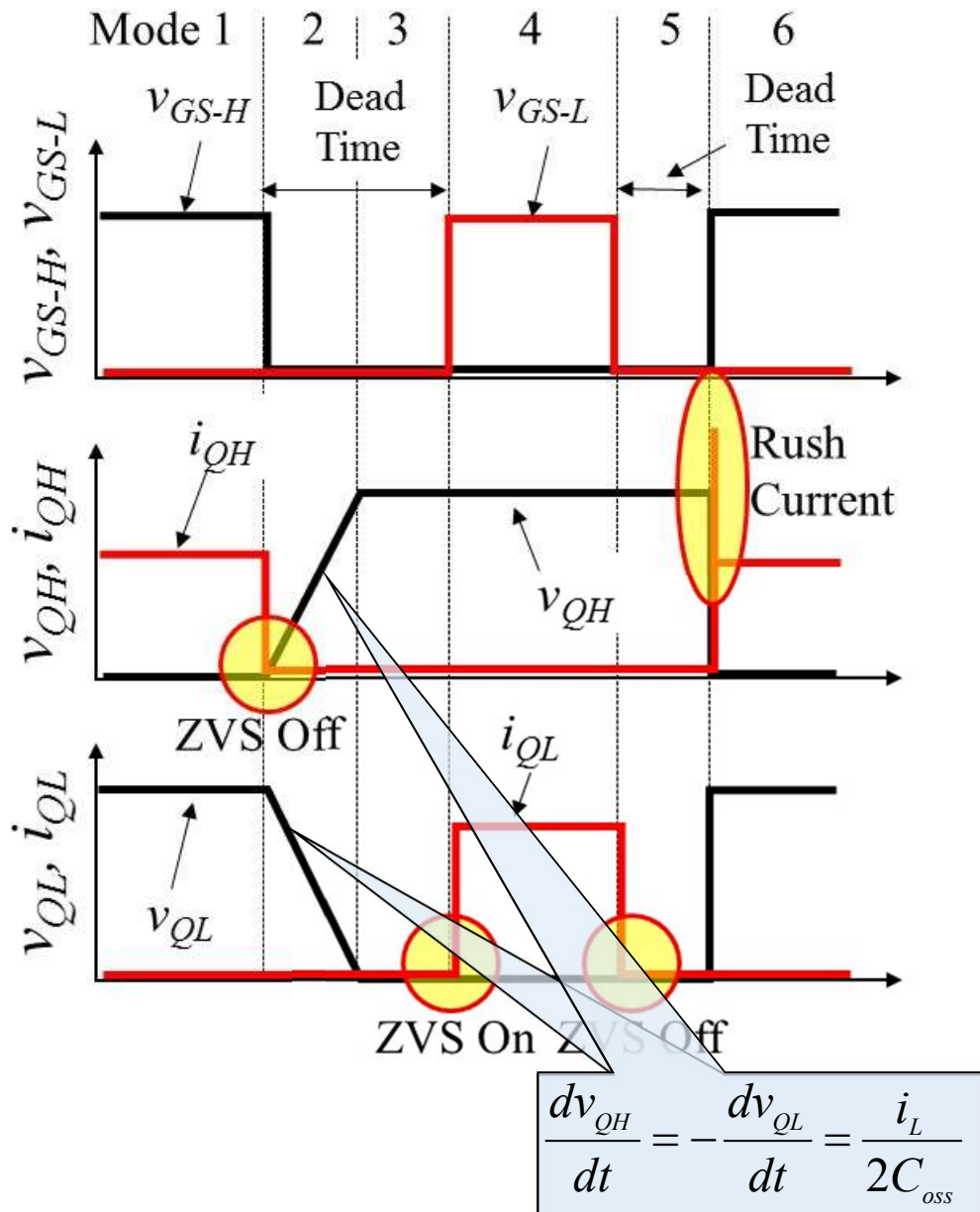


Mode 1

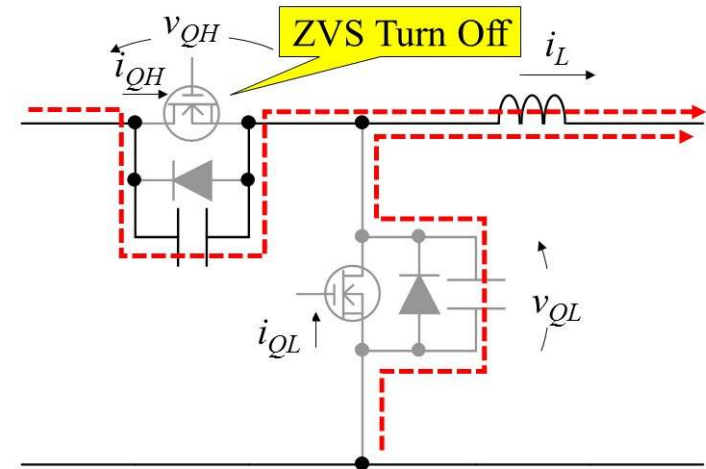


Mode 2

Switching Transitions of PWM Buck Converter

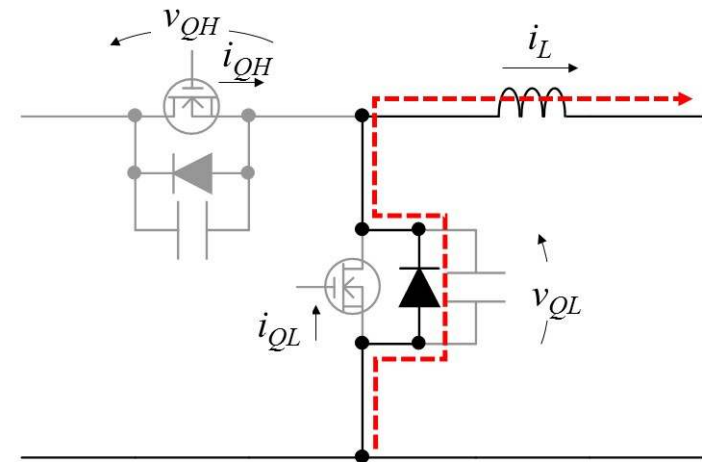
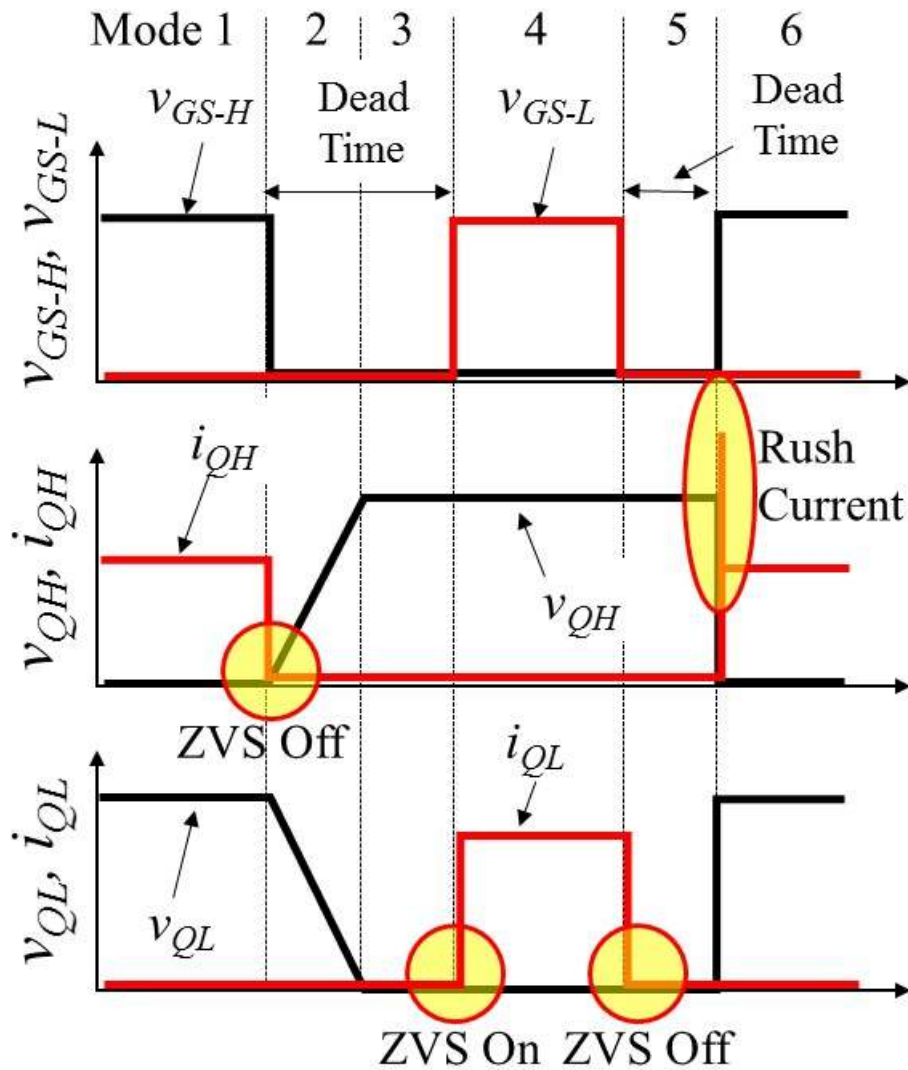


Mode 3

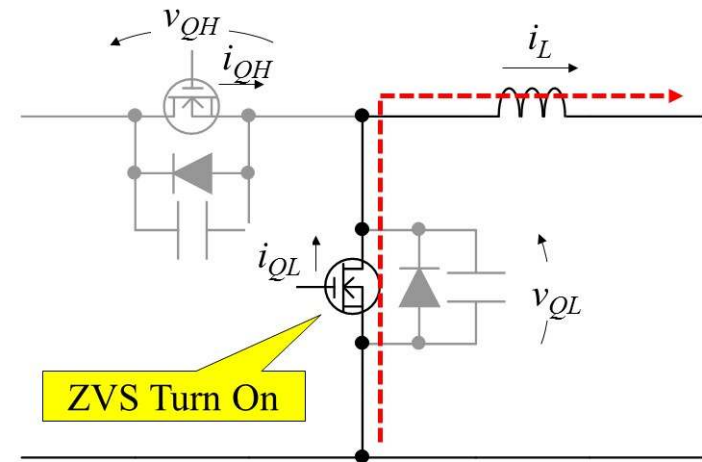


Mode 4

Switching Transitions of PWM Buck Converter

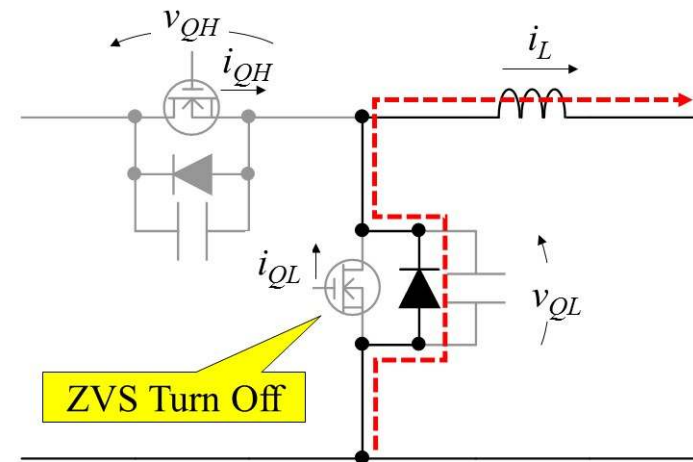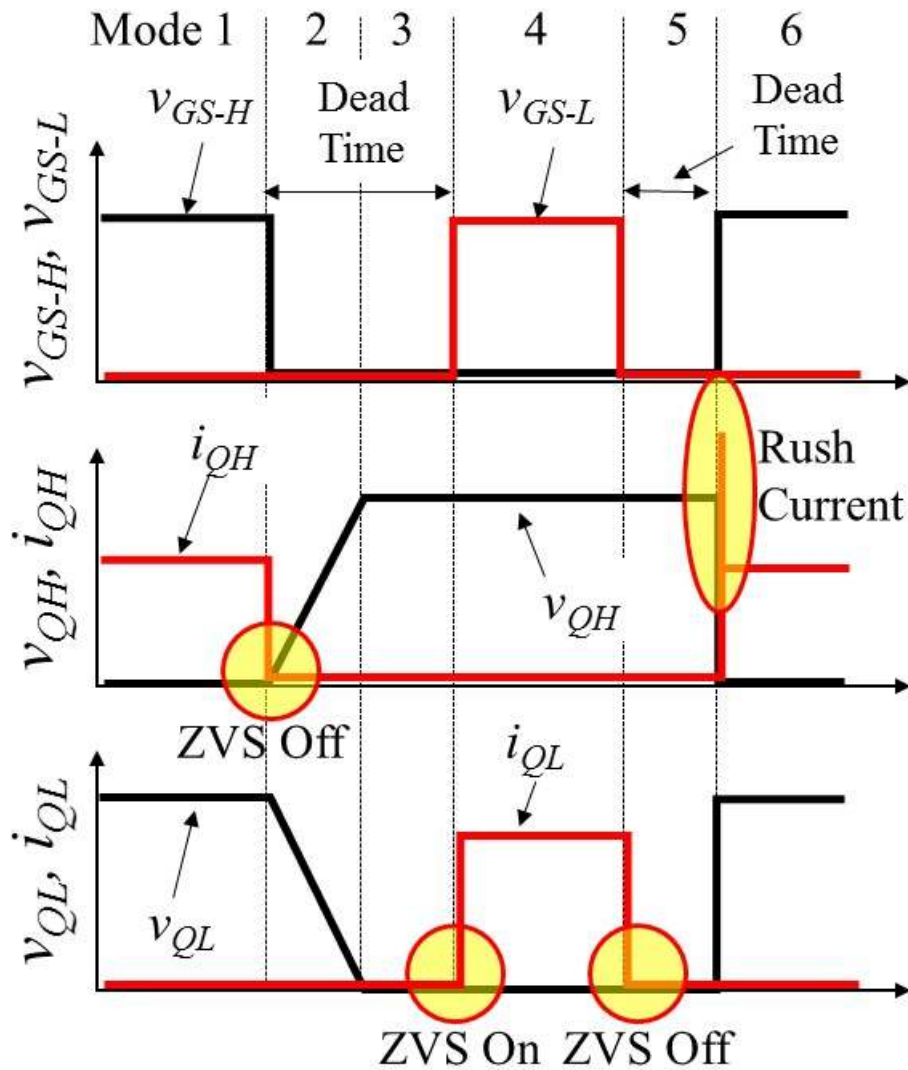


Mode 5

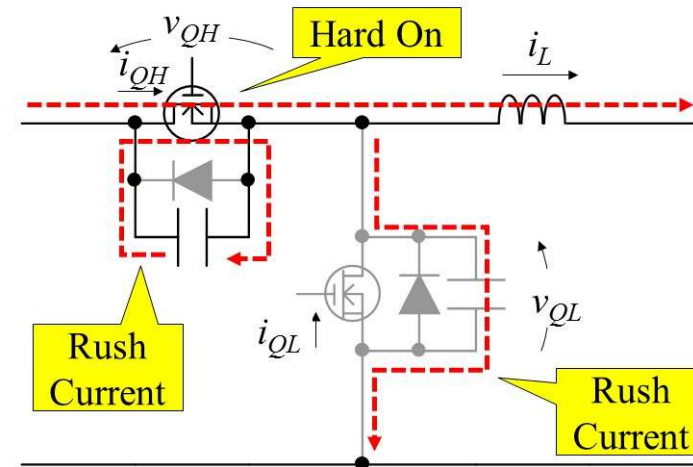


Mode 6

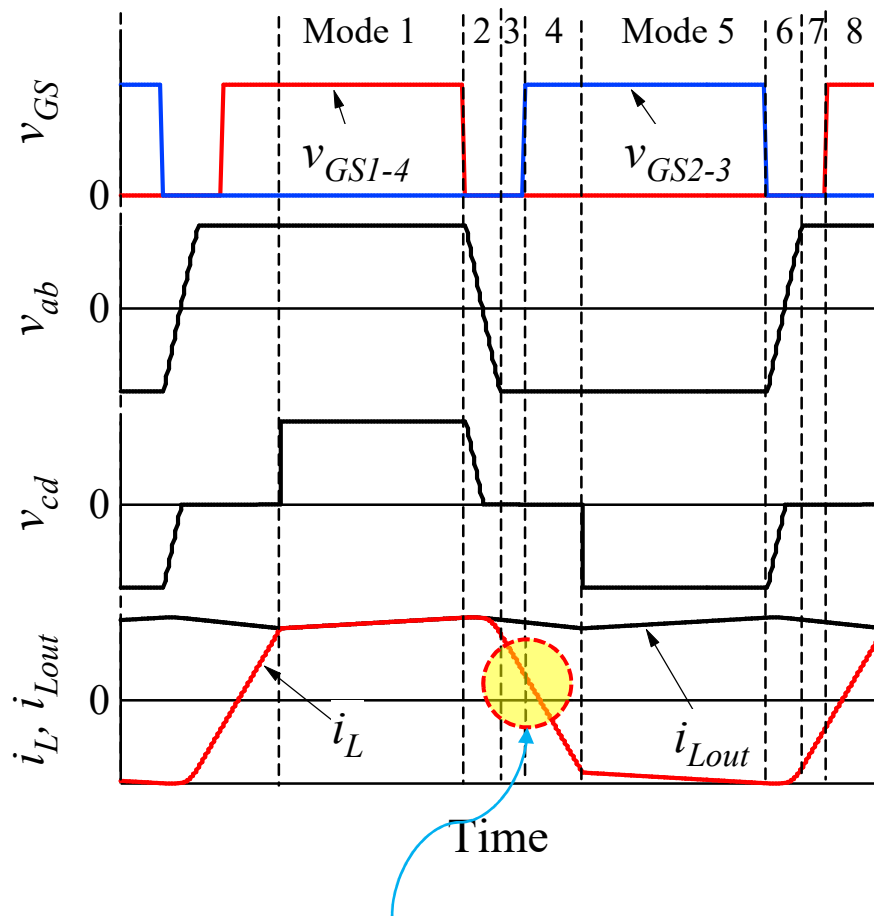
Key Waveforms and Current Flow Directions




Q₂ and Q₃ need to be turned on before i_L reaches zero

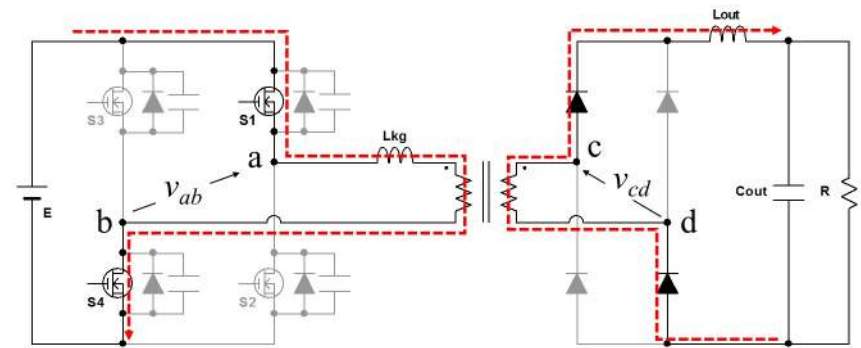

Mode 1


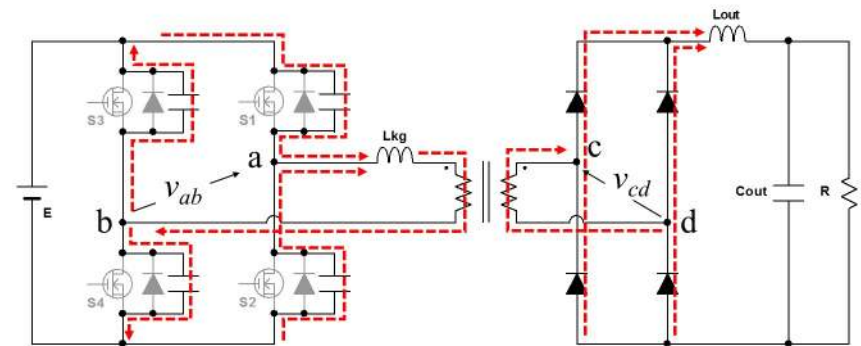


Mode 2

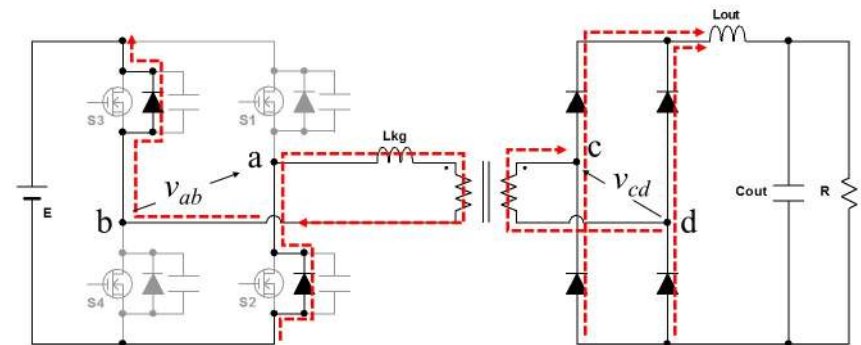


Mode 3

Key Waveforms and Current Flow Directions

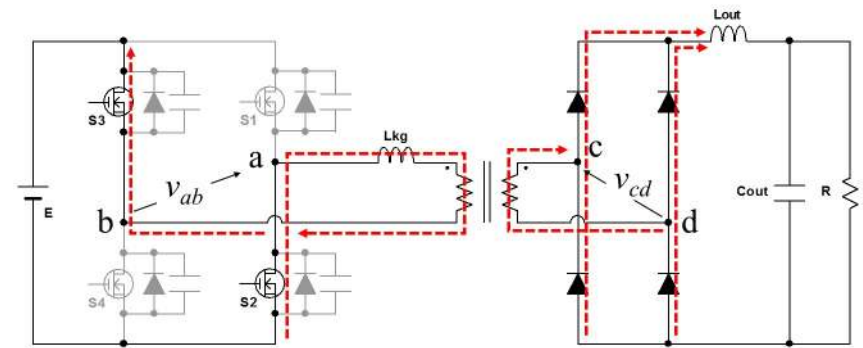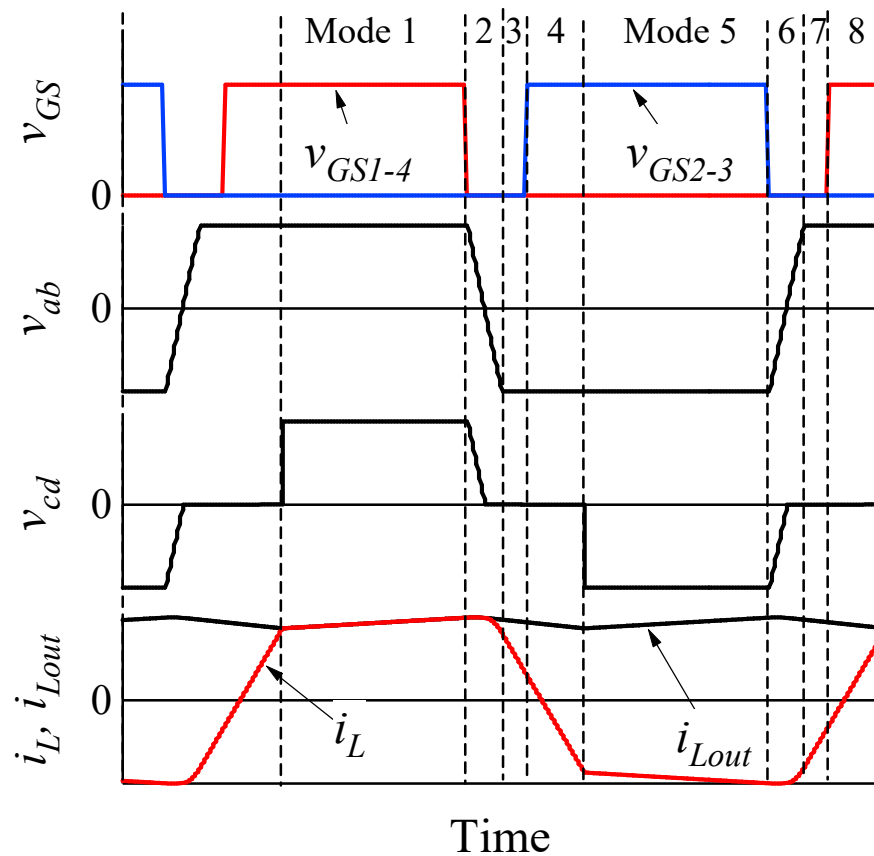

Mode 4

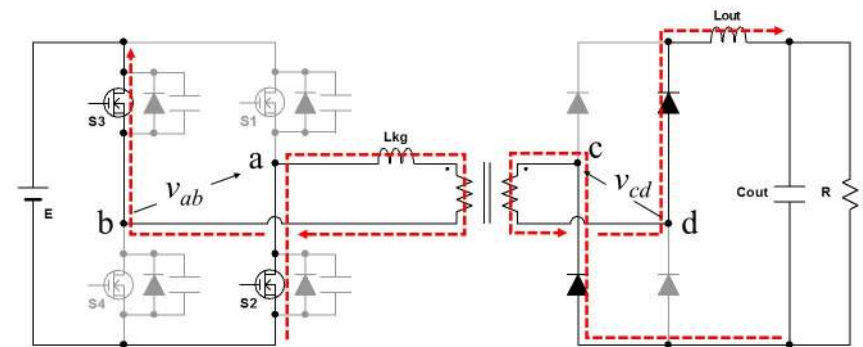

Mode 5

Modes 5–8 are symmetrical to Modes 1–4

Example: Failure in Soft Switching

